ab-lolt Basic Electricity & Electronics

Transistor Feedback Circuits

FACET®



Student Workbook

91567-00 Edition 4



FOURTH EDITION

Second Printing, March 2005

Copyright March, 2003 Lab-Volt Systems, Inc.

ISBN 0-86657-231-7

Lab-Volt[®] and F.A.C.E.T.[®] logos are trademarks of Lab-Volt Systems, Inc.

All other trademarks are the property of their respective owners. Other trademarks and trade names may be used in this document to refer to either the entity claiming the marks and names or their products. Lab-Volt System, Inc. disclaims any proprietary interest in trademarks and trade names other than its own.

All rights reserved. No part of this publication may be reproduced, stored in a retrieval system, or transmitted in any form by any means, electronic, mechanical, photocopied, recorded, or otherwise, without prior written permission from Lab-Volt Systems, Inc.

Information in this document is subject to change without notice and does not represent a commitment on the part of Lab-Volt Systems, Inc. The Lab-Volt[®] F.A.C.E.T.[®] software and other materials described in this document are furnished under a license agreement or a nondisclosure agreement. The software may be used or copied only in accordance with the terms of the agreement.

Lab-Volt License Agreement

By using the software in this package, you are agreeing to become bound by the terms of this License Agreement, Limited Warranty, and Disclaimer.

This License Agreement constitutes the complete agreement between you and Lab-Volt. If you do not agree to the terms of this agreement, do not use the software. Promptly return the F.A.C.E.T. Resources on Multimedia (CD-ROM) compact discs and all other materials that are part of Lab-Volt's F.A.C.E.T. product within ten days to Lab-Volt for a full refund or credit.

1. License Grant. In consideration of payment of the license fee, which is part of the price you paid for this Lab-Volt product, Lab-Volt, as Licensor, grants to you, the Licensee, a nonexclusive, nontransferable license to use this copy of the CD-ROM software with the corresponding F.A.C.E.T. Lab-Volt reserves all rights not expressly granted to the Licensee.

2. Ownership. As the Licensee, you own the physical media on which the CD-ROM is originally or subsequently recorded or fixed, but Lab-Volt retains title to and ownership of the software programs recorded on the original compact disc and any subsequent copies of the CD-ROM, regardless of the form or media in or on which the original and other copies may exist. This license is not a sale of the original software program of Lab-Volt's CD-ROM or any portion or copy of it.

3. Copy Restrictions. The CD-ROM software and the accompanying materials are copyrighted and contain proprietary information and trade secrets of Lab-Volt. Unauthorized copying of the CD-ROM even if modified, merged, or included with other software or with written materials is expressly forbidden. You may be held legally responsible for any infringement of Lab-Volt's intellectual property rights that is caused or encouraged by your failure to abide by the terms of this agreement. You may make copies of the CD-ROM solely for backup purposes provided the copyright notice is reproduced in its entirety on the backup copy.

4. Permitted Uses. This CD-ROM, Instructor's Guide, and all accompanying documentation is licensed to you, the Licensee, and may not be transferred to any third party for any length of time without the prior written consent of Lab-Volt. You may not modify, adapt, translate, reverse engineer, decompile, disassemble, or create derivative works based on the Lab-Volt product without the prior written permission of Lab-Volt. Written materials provided to you may not be modified, adapted, translated, or used to create derivative works without the prior written consent of Lab-Volt.

5. Termination. This agreement is effective until terminated. It will terminate automatically without notice from Lab-Volt if you fail to comply with any provisions contained herein. Upon termination you shall destroy the written materials, Lab-Volt's CD-ROM software, and all copies of them, in part or in whole, including modified copies, if any. **6. Registration.** Lab-Volt may from time to time update the CD-ROM. Updates can be made available to you only if a properly signed registration card is filed with Lab-Volt or an authorized registration card recipient.

7. Miscellaneous. This agreement is governed by the laws of the State of New Jersey.

Limited Warranty and Disclaimer

This CD-ROM software has been designed to assure correct operation when used in the manner and within the limits described in this Instructor's Guide. As a highly advanced software product, it is quite complex; thus, it is possible that if it is used in hardware configurations with characteristics other than those specified in this Instructor's Guide or in environments with nonspecified, unusual, or extensive other software products, problems may be encountered by a user. In such cases, Lab-Volt will make reasonable efforts to assist the user to properly operate the CD-ROM but without guaranteeing its proper performance in any hardware or software environment other than as described in this Instructor's Guide.

This CD-ROM software is warranted to conform to the descriptions of its functions and performance as outlined in this Instructor's Guide. Upon proper notification and within a period of one year from the date of installation and/or customer acceptance, Lab-Volt, at its sole and exclusive option, will remedy any nonconformity or replace any defective compact disc free of charge. Any substantial revisions of this product, made for purposes of correcting software deficiencies within the warranty period, will be made available, also on a licensed basis, to registered owners free of charge. Warranty support for this product is limited, in all cases, to software errors. Errors caused by hardware malfunctions or the use of nonspecified hardware or other software are not covered.

LICENSOR MAKES NO OTHER WARRANTIES OF ANY KIND CONCERNING THIS PRODUCT, INCLUDING WARRANTIES OR MERCHANTABILITY OR OF FITNESS FOR A PARTICULAR PURPOSE. LICENSOR DISCLAIMS ALL OBLIGATIONS AND LIABILITIES ON THE PART OF LICENSOR FOR DAMAGES, INCLUDING BUT NOT LIMITED TO SPECIAL OR CONSEQUENTIAL DAMAGES ARISING OUT OF OR IN CONNECTION WITH THE USE OF THE SOFTWARE PRODUCT LICENSED UNDER THIS AGREEMENT.

Questions concerning this agreement and warranty and all requests for product repairs should be directed to the Lab-Volt field representative in your area.

LAB-VOLT SYSTEMS, INC. P.O. Box 686 Farmingdale, NJ 07727 Attention: Program Development Phone: (732) 938-2000 or (800) LAB-VOLT Fax: (732) 774-8573 Technical Support: (800) 522-4436 Technical Support E-Mail: techsupport@labvolt.com

Table of Contents

Unit 1 – Introduction to the Circuit Board	1
Exercise 1 – Component Location and Identification	4
Exercise 2 – Feedback Amplifier Operation	5
Unit 2 – Series Feedback	7
Exercise 1 – Effect of Feedback on AC Gain	11
Exercise 2 – Effect of Feedback on Bandwidth	
Exercise 3 – Effect of Feedback on Impedance	13
Unit 3 – Shunt Feedback	15
Exercise 1 – Effect of Shunt Feedback on AC Gain	
Exercise 2 – Effect of Feedback on Bandwidth	19
Exercise 3 – Effect of Feedback on Impedance	
Unit 4 – Multistage Amplifier Feedback	23
Exercise 1 – Shunt-Series Current Gain	
Exercise 2 – Shunt-Series Output Impedance	27
Exercise 3 – Series-Shunt Voltage Gain	
Exercise 4 – Series-Shunt Output Impedance	
Unit 5 – Differential Amplifiers	
Exercise 1 – Operation	
Exercise 2 – Differential Gain	
Exercise 3 – Gain	
Appendix A – Safety	A-ii

Introduction

This Student Workbook provides a unit-by-unit outline of the Fault Assisted Circuits for Electronics Training (F.A.C.E.T.) curriculum.

The following information is included together with space to take notes as you move through the curriculum.

- The unit objective
- Unit fundamentals
- A list of new terms and words for the unit
- Equipment required for the unit
- The exercise objectives
- Exercise discussion
- Exercise notes

The Appendix includes safety information.

UNIT 1 – INTRODUCTION TO THE CIRCUIT BOARD

UNIT OBJECTIVE

At the completion of this unit, you will be able to locate and identify the major circuit blocks on the TRANSISTOR FEEDBACK CIRCUITS circuit board.

UNIT FUNDAMENTALS

The TRANSISTOR FEEDBACK CIRCUITS circuit board consists of 4 circuit blocks:

SERIES FEEDBACK/SHUNT FEEDBACK circuit block

MULTISTAGE SHUNT-SERIES FEEDBACK circuit block

MULTISTAGE SERIES-SHUNT FEEDBACK circuit block

DIFFERENTIAL AMPLIFIER circuit block.

A GENERATOR BUFFER circuit and an ATTENUATOR circuit are also included on the circuit board. Three of the circuit blocks introduce various **feedback** methods. The fourth circuit block is a **differential amplifier**.



The attenuator can be used to attenuate or reduce the magnitude of an input signal.



To become familiar with a feedback circuit on the TRANSISTOR FEEDBACK CIRCUITS circuit board, you will set up a typical circuit and use test equipment to look at its operation.

Two-post connectors allow circuit configuration changes and circuit power application.

NEW TERMS AND WORDS

feedback - the return of a portion of an amplifier's output to its input. *differential amplifier* - an amplifier whose output signal is proportional to the algebraic difference between two input signals. *attenuator* - a passive network that reduces the level of a signal.

EQUIPMENT REQUIRED

F.A.C.E.T. base unit Multimeter Oscilloscope, dual trace Generator, sine wave TRANSISTOR FEEDBACK CIRCUITS circuit board

Exercise 1 – Component Location and Identification

EXERCISE OBJECTIVE

When you have completed this exercise, you will be able to locate all major circuits on the TRANSISTOR FEEDBACK CIRCUITS circuit board. You will verify your results by correctly identifying circuits and their major components.

DISCUSSION

- The TRANSISTOR FEEDBACK CIRCUITS circuit board demonstrates four common forms of feedback.
- SERIES FEEDBACK/SHUNT FEEDBACK: Series and shunt feedback in a single transistor amplifier.
- MULTISTAGE SHUNT-SERIES FEEDBACK and MULTISTAGE SERIES-SHUNT FEEDBACK: Multistage circuits that contain two stages of amplification and use a combination of series and shunt feedback.
- DIFFERENTIAL AMPLIFIER: Two transistors in a circuit that amplifies small signals.

Exercise 2 – Feedback Amplifier Operation

EXERCISE OBJECTIVE

When you have completed this exercise, you will be able to set up and activate a typical circuit block by using two-post connectors and applying power. You will verify your results with an oscilloscope.

DISCUSSION

- The SERIES FEEDBACK/SHUNT FEEDBACK circuit block develops series and shunt feedback in an amplifier circuit.
- The feedback is in parallel with (shunted across) the amplifier input.
- Demonstrate amplifier gain reduction with the use of negative feedback.

UNIT 2 – SERIES FEEDBACK

UNIT OBJECTIVE

At the completion this unit, you will be able to describe the effect of a series feedback circuit by using ac and dc measurements.

UNIT FUNDAMENTALS



Degenerative feedback also known as inverse feedback or negative feedback, is produced when a portion of an amplifier's output signal is transferred to and opposes the effect of the input.



Negative feedback decreases the gain, increases the bandwidth, and affects the **input impedance** and the **output impedance** of an amplifier. **Series feedback** is applied in series with the input (V_a) .

Current feedback is a feedback current that is proportional to output current (I_{RCL}).



The output current (I_{RCL}) flows through the emitter feedback resistor (R_E).

I_{RCL} through R_E develops a feedback voltage (V_f).

 V_f opposes the input voltage (V_a).



The feedback ratio (β) is the fractional part of the output voltage that is fed back to the input.



To understand the feedback ratio (β) in a common emitter amplifier such as this one, consider the output taken across the emitter resistor (R_E).

Since all of the output voltage (V_0) is fed back to the input ($V_f = V_0$), the feedback ratio (β) would be 1.

The gain relationship for any type of amplifier with feedback is determined by the following equation, where A_f is the gain with feedback and A is the gain without feedback.

 $H_{f} = \frac{H}{1 + (H \times B)}$

In case of negative feedback, β is a negative quantity, and you need to take the minus sign into account when you calculate gain.

NEW TERMS AND WORDS

degenerative feedback - a mode of feedback in which a portion of the output is fed back to and opposes the input; also called inverse feedback or negative feedback.

input impedance - the impedance across the input terminals of an amplifier.

output impedance - the impedance across the output terminals of an amplifier; also called source impedance.

series feedback - a feedback signal applied in series with the input signal.

current feedback - a feedback signal that is proportional to output current.

feedback ratio - the portion of the output voltage that is fed back to the input; also referred to as feedback factor.

EQUIPMENT REQUIRED

F.A.C.E.T. base unit Multimeter Oscilloscope, dual trace Generator, sine wave TRANSISTOR FEEDBACK CIRCUITS circuit board

Exercise 1 – Effect of Feedback on AC Gain

EXERCISE OBJECTIVE

When you have completed this exercise, you will be able to describe and measure the effect of series feedback on ac gain by using a typical series feedback circuit. You will verify your results with a multimeter and an oscilloscope.

DISCUSSION

- A common emitter type amplifier with an unbypassed emitter resistor is used to demonstrate series feedback, a common type of negative feedback.
- Negative feedback results in a reduction in gain of the amplifier to which it is applied.
- Assume an increase in base current from a positive-going input signal: voltage at the emitter will go more positive, effectively reducing the base signal by an equal amount.
- A large capacitor across the emitter resistor effectively bypasses the positive-going input signal to ground so that no reduction of the base signal occurs.
- The feedback factor (β) is determined from the values of the emitter resistor (R_E) and the collector resistor (R_C).
- To achieve negative feedback, the feedback factor (β) must be a negative quantity.

Exercise 2 – Effect of Feedback on Bandwidth

EXERCISE OBJECTIVE

When you have completed this exercise, you will be able to under-stand the effect of series negative feedback on bandwidth by using a typical series feedback circuit. You will verify your results with an oscilloscope.

DISCUSSION

- Amplifier bandwidth defined
- Lower and upper cutoff frequencies specified as 3 dB down from midrange level
- Approximate bandwidth using square wave input signal and formula fx = 0.159/T.

Negative feedback reduces the gain of an amplifier and increases bandwidth.

Exercise 3 – Effect of Feedback on Impedance

EXERCISE OBJECTIVE

When you have completed this exercise, you will be able to describe the effect of series feedback on input impedance by using a typical series feedback circuit. You will verify your results with an oscilloscope.

DISCUSSION

- Simple input impedance is the sum of all series elements and the transistor base input impedance including effects of any bias resistors.
- Adding series negative feedback to a common emitter amplifier increases input impedance.
- $V_{R1} = V_i V_b$
- $I_i = V_{R1}/R1$
- $Z_i = V_i/I_i$

UNIT 3 – SHUNT FEEDBACK

UNIT OBJECTIVE

At the completion of this unit, you will be able to describe the effects of shunt feedback on ac gain, bandwidth, input impedance, and output impedance by using a typical shunt feedback circuit.

UNIT FUNDAMENTALS



Shunt negative feedback places a portion of an amplifier's output voltage in shunt (parallel) with the input voltage.

Shunt feedback effectively shunts the input and the output of an amplifier.



For a transistor amplifier without feedback, the gain (A) depends on the transistor ac gain (β). For the transistor used in this circuit, β can vary from 50 to 300.

 $Av = \beta$



The gain (A_f) of a shunt feedback amplifier equals the ratio of the feedback resistor (R_f) to the series input resistor (R_i) .

$$A_f = R_f / R_i$$

For shunt feedback, the feedback ratio (β) is the reciprocal of A_f.

$$\beta = R_i / R_f$$

Therefore, this equation applies.

$$\beta = 1/A_f$$

Negative shunt feedback decreases gain but increases the bandwidth.

NEW TERMS AND WORDS

Shunt feedback - feedback voltage that is effectively applied in parallel with the input signal.

EQUIPMENT REQUIRED

F.A.C.E.T. base unit Multimeter Oscilloscope, dual trace Generator, sine/square wave TRANSISTOR FEEDBACK CIRCUITS circuit board

Exercise 1 – Effect of Shunt Feedback on AC Gain

EXERCISE OBJECTIVE

When you have completed this exercise, you will be able to understand the effect of shunt negative feedback on ac gain by using a typical shunt feedback circuit. You will verify your results with an oscilloscope.

EXERCISE DISCUSSION

- A small positive change in V_i of a transistor increases base current which, in turn, decreases collector voltage V_c.
- A portion of this decreasing collector voltage is sent back to, and summed with, the rising input signal.
- The positive-going voltage V_i and the opposite-in-phase V_c oppose each other.
- The gain with feedback (A_f) of a shunt feedback amplifier is approximately equal to the ratio of feedback resistor R_f to series input resistor R_i : $A_f = R_f/R_i$.
- For shunt feedback, the feedback ratio (β) is the reciprocal of Af: $\beta = R_i/R_f$.

Exercise 2 – Effect of Feedback on Bandwidth

EXERCISE OBJECTIVE

When you have completed this exercise, you will understand the effect of shunt negative feedback on bandwidth by using a typical shunt feed-back circuit. You will verify your results with an oscilloscope.

DISCUSSION

- Bandwidth defines the breadth of input frequency for which the output amplitude remains constant, within prescribed limits
- Limits are usually defined as upper and lower cutoff frequency
- Cutoff frequency is where the gain of an amplifier falls to 3 dB of its average gain
- Average gain means the midrange gain: the gain at the center of its bandwidth
- A square wave can be used to measure bandwidth of an amplifier by checking certain characteristics of the square wave at the output of the amplifier
- As viewed on an oscilloscope, the lower cutoff frequency is the time (T) it takes the squarewave leading edge to reach 63 percent of its final level
- As viewed on an oscilloscope, the upper cutoff frequency is the time it takes the output to fall 63 percent
- Simplified equation for lower (or upper) cutoff frequency is: f1 (or f2) = 0.159/T

Exercise 3 – Effect of Feedback on Impedance

EXERCISE OBJECTIVE

When you have completed this exercise, you will understand the effect of shunt negative feedback on input and output impedance by using a typical shunt feedback circuit. You will verify your results with an oscilloscope.

DISCUSSION

- Bandwidth defines the breadth of input frequency for which the output amplitude remains constant, within prescribed limits
- Limits are usually defined as upper and lower cutoff frequency
- Cutoff frequency is where the gain of an amplifier falls to 3 dB of its average gain
- Average gain means the midrange gain: the gain at the center of its bandwidth
- A square wave can be used to measure bandwidth of an amplifier by checking certain characteristics of the square wave at the output of the amplifier
- As viewed on an oscilloscope, the lower cutoff frequency is the time (T) it takes the squarewave leading edge to reach 63 percent of its final level
- As viewed on an oscilloscope, the upper cutoff frequency is the time it takes the output to fall 63 percent
- Simplified equation for lower (or upper) cutoff frequency is: f1 (or f2) = 0.159/T

UNIT 4 – MULTISTAGE AMPLIFIER FEEDBACK

UNIT OBJECTIVE

At the completion of this unit, you will be able to describe the operation and characteristics of two types of multistage feedback amplifiers by using ac and dc measurements.

UNIT FUNDAMENTALS

Multistage feedback is in an amplifier circuit that has more than one stage. This feedback is across the entire amplifier circuit.

There are two basic types of multistage amplifier feedback: shunt-series and series-shunt.



Shown is a shunt-series feedback circuit. Resistor R_{sh} provides shunt feedback to the input stage.

Resistor Ref provides series feedback to the output stage.

In a multistage amplifier with shunt-series feedback, the feedback ratio of R_{sh}/R_{ef} determines the ac current gain (Ai = R_{sh}/R_{ef}).



Shown is a series-shunt feedback circuit.

Resistor Ref provides series feedback to the input stage.

Resistor R_{sh} provides shunt feedback to the output stage.

In a series-shunt multistage amplifier, the feedback ratio of R_{sh}/R_{ef} determines the voltage gain $(Av = R_{sh}/R_{ef})$.

NEW TERMS AND WORDS

shunt-series - a multistage amplifier in which the input stage has shunt feedback. *series-shunt -* a multistage amplifier in which the input stage has series feedback. *constant current source -* a high impedance source that delivers the same load current

EQUIPMENT REQUIRED

F.A.C.E.T. base unit Multimeter Oscilloscope, dual trace Generator, sine wave TRANSISTOR FEEDBACK CIRCUITS circuit board

Exercise 1 – Shunt-Series Current Gain

EXERCISE OBJECTIVE

When you have completed this exercise, you will be able to calculate and measure shunt-series current gain by using a typical shunt-series multistage amplifier circuit. You will verify your results with an oscilloscope.

DISCUSSION

• Known as a current amplifier, current gain (Ai) equals the shunt resistance (R_{sh}) divided by the series resistance (R_{ef}) .

Exercise 2 – Shunt-Series Output Impedance

EXERCISE OBJECTIVE

When you have completed this exercise, you will be able to measure shunt-series output impedance by using a typical shunt-series multi-stage amplifier circuit. You will verify your results with an oscilloscope and a multimeter.

DISCUSSION

- Circuit output impedance (Zo) equals the transistor collector impedance in parallel with the collector resistor.
- $Zo = (Rco \times Rc)/(Rco + Rc)$
- Because of the high output impedance of the circuit, it acts as a constant current source for small loads.

Exercise 3 – Series-Shunt Voltage Gain

EXERCISE OBJECTIVE

When you have completed this exercise, you will be able to calculate and measure series-shunt voltage gain by using a typical series-shunt multistage amplifier circuit. You will verify your results with an oscilloscope.

DISCUSSION

- In a multistage amplifier with series-shunt feedback, resistor R_{ef} provides series feedback and R_{sh} provides shunt feedback to the input stage
- Circuit voltage gain is directly related to and R_{sh}
- $Av = R_{sh}/R_{ef}$
- A series-shunt feedback amplifier has high voltage gain

Exercise 4 – Series-Shunt Output Impedance

EXERCISE OBJECTIVE

When you have completed this exercise, you will be able to measure the output impedance of a series-shunt feedback amplifier by using a variable load connected to the circuit output. You will verify your results with an oscilloscope and a multimeter.

DISCUSSION

- Output impedance of a series-shunt amplifier equals the shunt resistor divided by the transistor beta in parallel with the collector resistor
- $Zo = R_{sh}/\beta \parallel Rc$

UNIT 5 – DIFFERENTIAL AMPLIFIERS

UNIT OBJECTIVE

At the completion of this unit, you will be able to describe the operation of a differential amplifier by using ac and dc measurements.

UNIT FUNDAMENTALS



This circuit is a **differential amplifier**. It has two transistors (Q1 and Q2) with equal gains.

The two emitter resistors (R4A and R4B) are tied together and connect to a common emitter resistor (R5). R5 sets the circuit operating current, which divides equally between the two transistors.



A differential amplifier has several modes of opera-tion. You can take the output between the two collectors or from either transistor collector to ground.

The output taken from one collector with respect to ground is called a **single-ended output**. The output taken between the two collectors is called a **double-ended output**, or more commonly, a **differential output**.

A differential amplifier can also have a **single-ended input** signal at either input or a **differential input**, which is applied between he two inputs and is not referenced to ground.

NEW TERMS AND WORDS

differential amplifier - an amplifier whose output signal is proportional to the algebraic difference between two input signals.

single-ended output - an output that is referenced to ground or circuit common.

differential output - an output circuit in which the signal is taken between two levels which are floating; there is no ground (common) reference.

single-ended input - an input that is referenced to ground or circuit common.

differential input - an input circuit that amplifies the difference between two input terminals.

EQUIPMENT REQUIRED

F.A.C.E.T. base unit Multimeter Oscilloscope, dual trace Generator, sine wave TRANSISTOR FEEDBACK CIRCUITS circuit board

Exercise 1 – Operation

EXERCISE OBJECTIVE

When you have completed this exercise, you will be able to describe some characteristics of a differential amplifier by using a typical differential circuit. You will verify your results with an oscilloscope and a multimeter.

DISCUSSION

- Differential amplifier is balanced to equalize collector voltage to zero.
- This circuit is a single-ended input with ground reference
- A single-ended in-phase output is taken from Q2
- A single-ended out-of-phase is taken from Q1
- A nonground-referenced differential output is taken from Q1/Q2 collectors.

Exercise 2 – Differential Gain

EXERCISE OBJECTIVE

When you have completed this exercise, you will be able to measure single-ended and differential gain by using a typical differential amplifier circuit. You will verify your results with an oscilloscope and a multimeter.

DISCUSSION

- Collector-to-emitter resistor-ratio determines the gain of each half of the differential amplifier
- $A = R_C/(2 \times R_E)$

Exercise 3 – Gain

EXERCISE OBJECTIVE

When you have completed this exercise, you will be able to measure common mode gain by using a typical differential amplifier circuit. You will verify your results with an oscilloscope, a signal generator, and a multimeter.

EXERCISE DISCUSSION

- A signal applied to both inputs $(V_{i1} \text{ and } V_{i2})$ at the same time is called a common mode signal.
- A characteristic of the differential amplifier is its ability to reject common mode signals.
- Common mode signals are rejected only at the differential output; the single-ended outputs contain the common mode signals.

APPENDIX A – SAFETY

Safety is everyone's responsibility. All must cooperate to create the safest possible working environment. Students must be reminded of the potential for harm, given common sense safety rules, and instructed to follow the electrical safety rules.

Any environment can be hazardous when it is unfamiliar. The F.A.C.E.T. computer-based laboratory may be a new environment to some students. Instruct students in the proper use of the F.A.C.E.T. equipment and explain what behavior is expected of them in this laboratory. It is up to the instructor to provide the necessary introduction to the learning environment and the equipment. This task will prevent injury to both student and equipment.

The voltage and current used in the F.A.C.E.T. Computer-Based Laboratory are, in themselves, harmless to the normal, healthy person. However, an electrical shock coming as a surprise will be uncomfortable and may cause a reaction that could create injury. The students should be made aware of the following electrical safety rules.

- 1. Turn off the power before working on a circuit.
- 2. Always confirm that the circuit is wired correctly before turning on the power. If required, have your instructor check your circuit wiring.
- 3. Perform the experiments as you are instructed: do not deviate from the documentation.
- 4. Never touch "live" wires with your bare hands or with tools.
- 5. Always hold test leads by their insulated areas.
- 6. Be aware that some components can become very hot during operation. (However, this is not a normal condition for your F.A.C.E.T. course equipment.) Always allow time for the components to cool before proceeding to touch or remove them from the circuit.
- 7. Do not work without supervision. Be sure someone is nearby to shut off the power and provide first aid in case of an accident.
- 8. Remove power cords by the plug, not by pulling on the cord. Check for cracked or broken insulation on the cord.